

## FUZZ AMPLIFIER

This is a classic design using an inverting amplifier with diodes in the feedback loop. A potential divider creates a phantom 0v rail for the non-inverting input.

