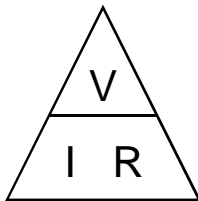


Formulas


Transformer ratios

$$\frac{\text{Primary voltage}}{\text{Secondary voltage}} = \frac{\text{primary winding}}{\text{secondary winding}}$$


Ohms Law



Power Law

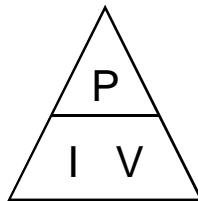

Charge

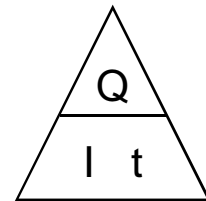

Frequency

$$t = \frac{1}{f}$$


t = cycle time
f = frequency

Ripple Voltage

$$V_r = \frac{I t}{C}$$

t = cycle time
C = capacitance

AC voltage

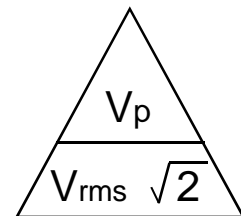

Transistor current

$$I_e = I_b + I_c$$

Transistor gain

$$I_c = I_b \ hfe$$


Transistor voltage

$$V_b = V_e + 0.7$$

ELECTRONICS A-LEVEL - POWER SUPPLY UNIT ASSESSMENT


Answer all questions.
Do not write on this paper. Provide your answers on a blank sheet of lined or plain paper.
When producing drawings and diagrams, use a sharp pencil and ruler where appropriate.

Question 1

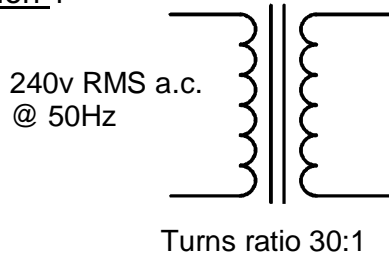

On the left is an a.c. transformer with a primary and secondary winding. They have a ratio of 30:1. The transformer primary is connected to a 240v a.c. supply whose frequency is 50 Hertz.

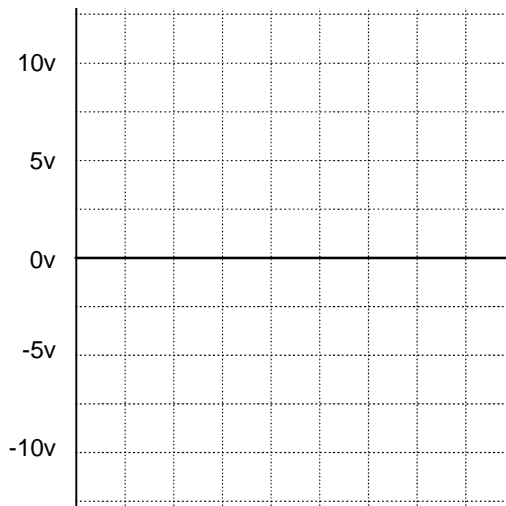
- a) Calculate the RMS voltage in the secondary winding. [1]
- b) Calculate the peak voltage in the secondary winding. [1]
- c) Calculate the cycle time of the secondary a.c. voltage [1]
- d) Copy out the grid below and draw the wave you expect to see on the secondary winding. [2]



X axis: 5ms per division

Y axis: 2.5 volts per division


A diode is added as shown

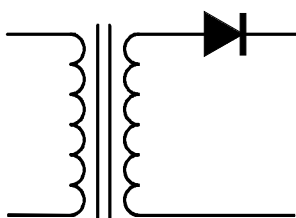

- e) What effect will the diode have on the peak voltage? [1]
- f) Draw on the same grid as d) the wave you would expect to see with the diode added. [2]

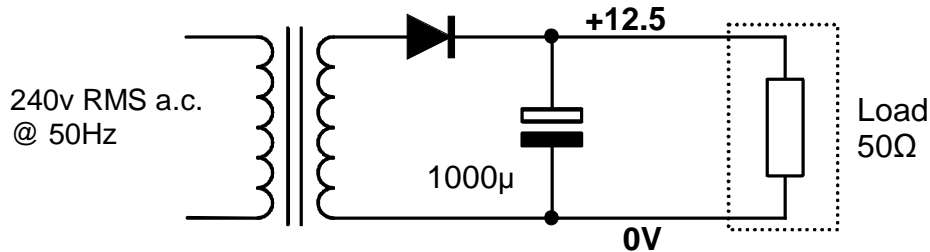Question 2

A supply is connected as shown. It has a secondary voltage rated at 12.5 volts and is smoothed using a $1000\mu\text{F}$ capacitor. This can be measured at +V. Connected to the supply is a load of $50\ \Omega$.




With the load connected,

- calculate the current flowing through the load resistance. [1]
- calculate the ripple voltage. [1]
- How could you reduce the ripple voltage? [1]

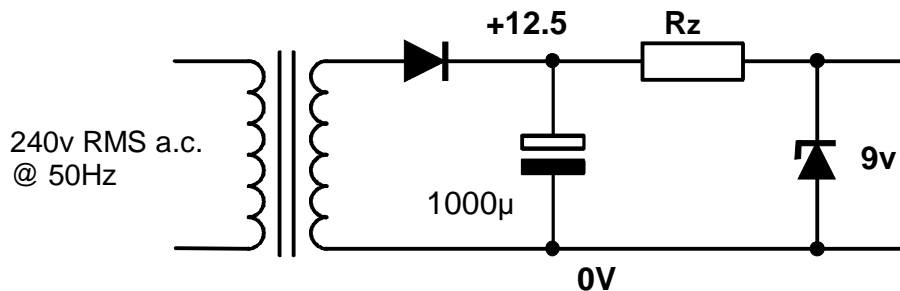Question 3


The load is removed and a 9 volt zener diode regulator is added as shown below.



- What does the zener diode do? [1]
- This supply must be capable of producing a maximum of 20mA at 9v. What value must resistor R_z have? [1]
- Calculate the power dissipated in the zener diode when there is no load connected [1]
- Redraw the circuit diagram of the supply using an NPN transistor to improve the current capability of the supply. [2]


Question 4

- a) Copy out the graph to the right. Draw out the current-voltage characteristics of a zener diode. [2]
- b) On your diagram, indicate where the breakdown point is. [1]
- c) What is meant by 'reverse bias'? [1]

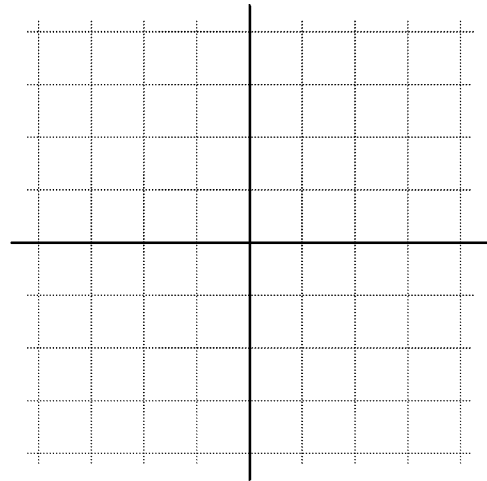

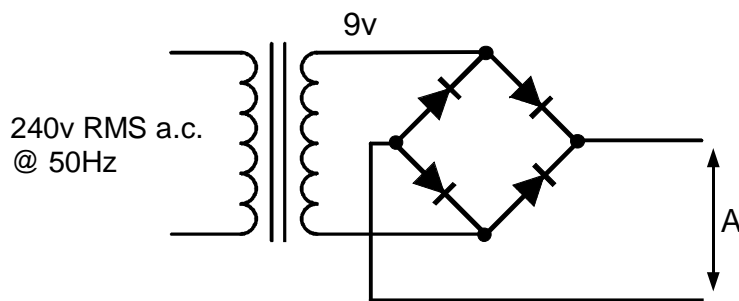Question 5

Below is a transformer with a bridge rectifier connected. The secondary voltage is 9 volts RMS.



- a) What is the peak voltage you would expect to see across point A? [1]
- b) Why are bridge rectifiers a more efficient way of rectifying a.c. waves rather than using just one diode? [1]
- c) Draw the approximate shape of the wave you would expect to see at point A. [1]
- d) What is meant by the term – split power supply? [1]
- e) Draw a circuit diagram of a split power supply. The output must be rectified and smoothed. [3]

End of test.