

NON-INVERTING AUDIO AMPLIFIER

This circuit uses an operational amplifier but overcomes the need for a split power supply. It uses a standard non-inverting amplifier circuit with some decoupling capacitors on the inputs and outputs.

$$\text{Gain} = R_f / R_{in} = 10$$

$$\text{Max Input} = 200\text{mV}$$

