

DUAL DIGIT COUNTER - Ver 1.3

Designed by Phil Townshend 2008

This is a basic up/down counter for 2 7-segment common cathode displays. Supply voltage can be from 5 to 15 volts but the resistors R5-18 will need to be increased for higher voltages to prevent damage to the driver ICs.

