

# 24 HOUR CLOCK

This circuit uses 4 bit binary counters and decoders to display the time and has 13 ICs.

