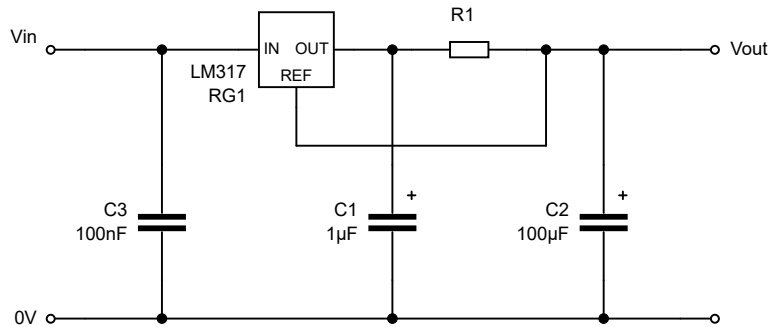


## CONSTANT CURRENT GENERATOR

This circuit uses the LM317 voltage regulator. Normally this regulator works using a reference voltage  $V_{ref}$ , of 1.25v between the output and the adjustment terminals. This combined with an external resistor, normally 240ohms, regulates it's output according to the formula:

$$V_o = V_{ref} \times 1 + (R_2/R_1), \quad (\text{ignoring } I_{adj} \text{ error})$$

$V_{ref}$  can also be used to control the current in the output by adjusting its voltage to achieve the required current flow through  $R_1$ .



The current is found using:

$$I_{out} = V_{ref} / R_1$$

So for a charge current of 500mA:

$$R_1 = V_{ref} / I_{out} = 1.25 / 0.5 = 2.5 \text{ ohms}$$

Other current can be set up to the maximum current rating of the regulator. The LM317T will provide about 1.5Amps and LM317K around 5Amps, but you must use a heatsink. Also the supply to the charger must be carefully chosen to insure minimal power loss through heat in the regulator.

Phil Townshend  
[www.edutek.ltd.uk](http://www.edutek.ltd.uk)