

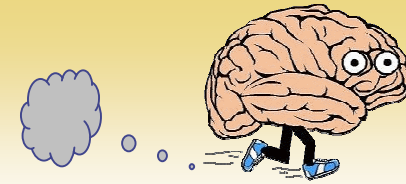
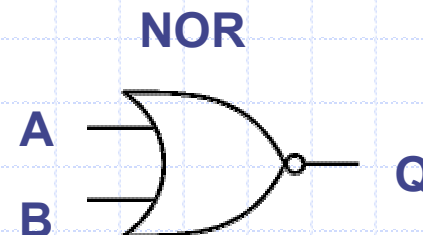
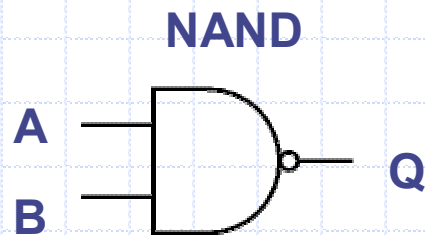
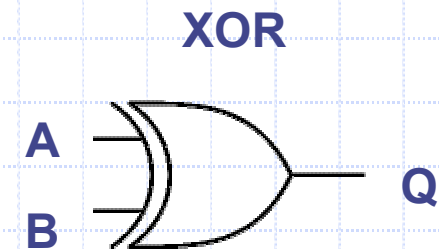


# QUIK THINKAZ

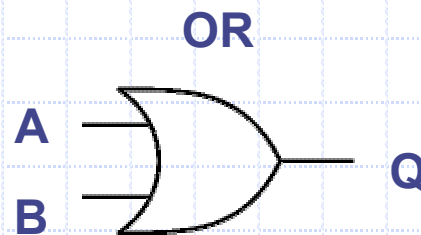


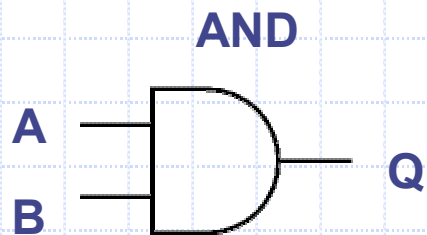FILL IN THE LOGIC TABLE FOR THE FOLLOWING GATES.








A	B	AND	OR	XOR	NAND	NOR
0	0					
0	1					
1	0					
1	1					

# QUIK THINKAZ

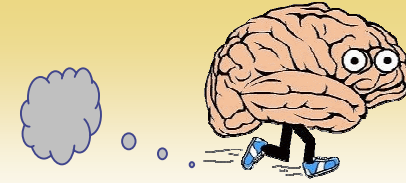

ANSWERS:

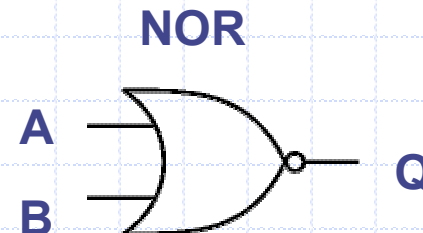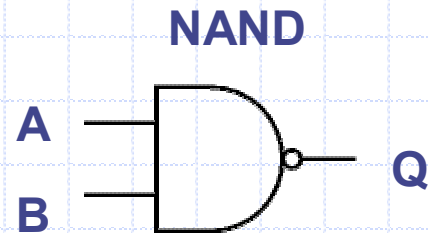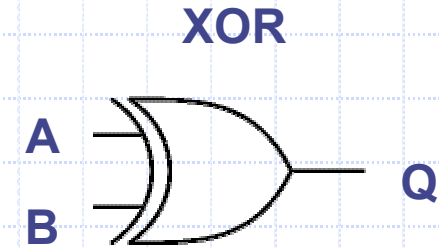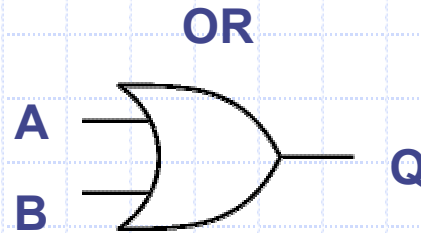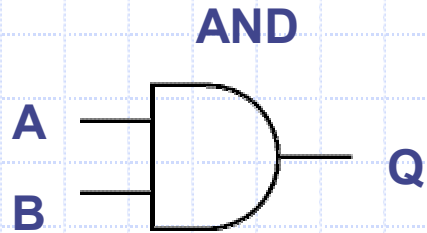

A	B	AND	OR	XOR	NAND	NOR
0	0	0	0	0	1	1
0	1	0	1	1	1	0
1	0	0	1	1	1	0
1	1	1	1	0	0	0