

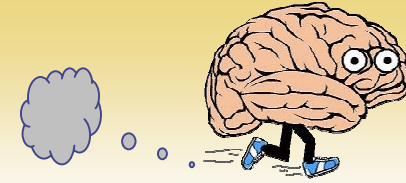
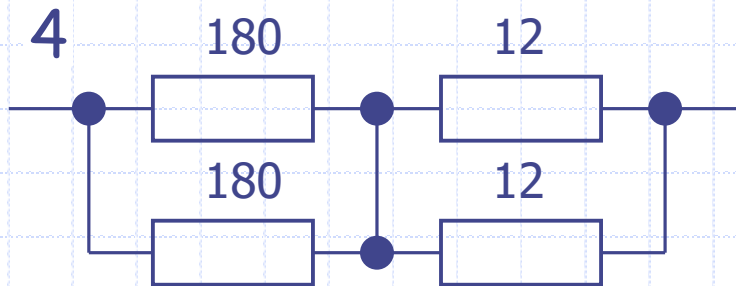
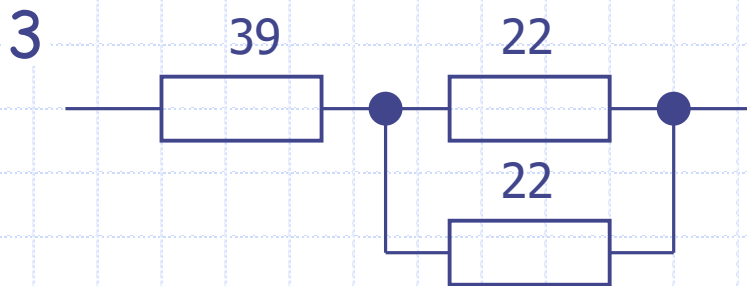


QUIK THINKAZ

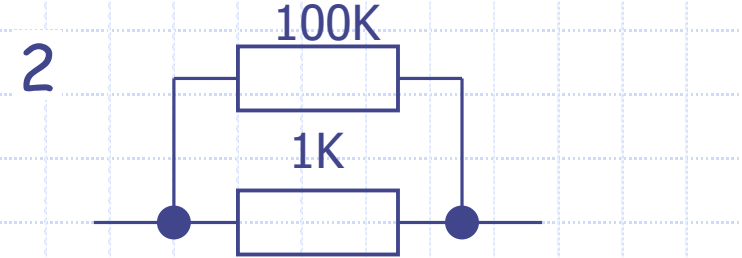

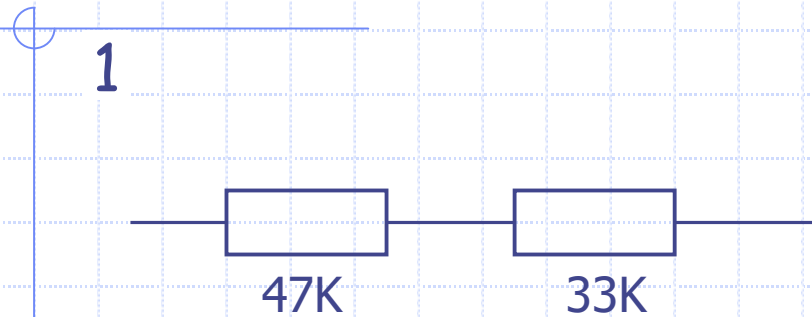
What is the total value of each resistor network?




Resistors in series: $R_t = R_1 + R_2$

Resistors in parallel: $R_t = \frac{R_1 \times R_2}{R_1 + R_2}$




QUIK THINKAZ

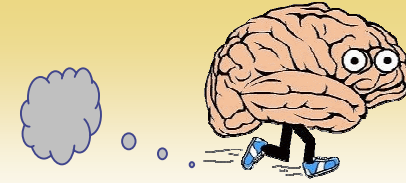

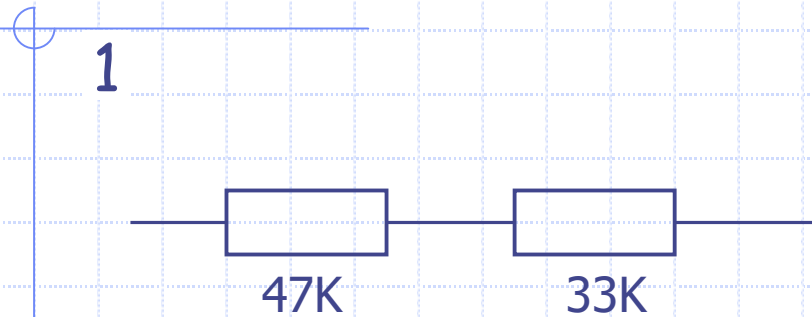
What is the overall value of each resistor network?



$$R_t = 47K + 33K = \mathbf{80K}$$

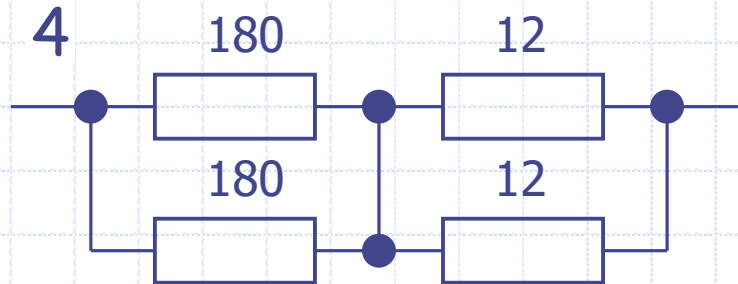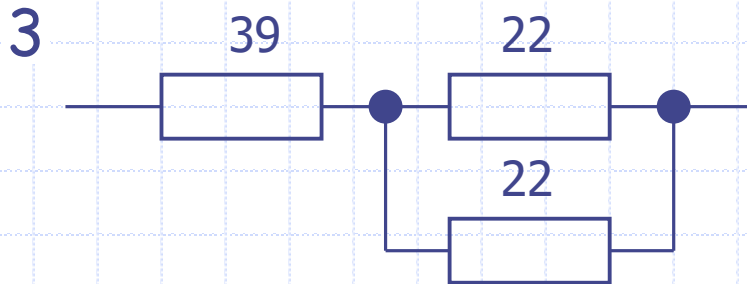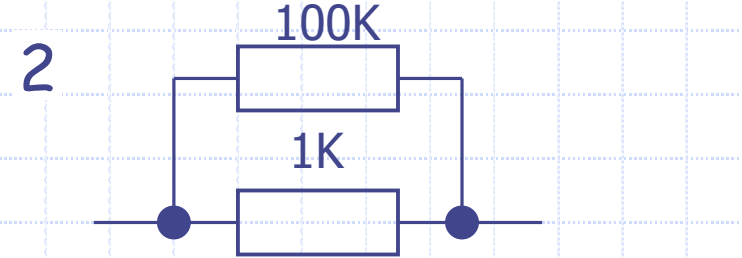


QUIK THINKAZ

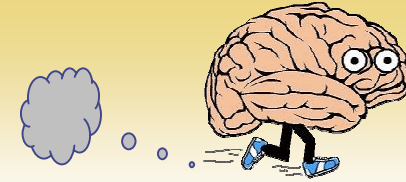


What is the overall value of each resistor network?

1

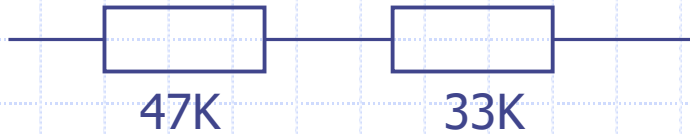


$$R_t = 47K + 33K = \mathbf{80K}$$

2

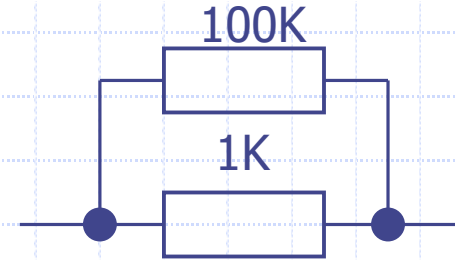


$$R_t = \frac{100K \times 1K}{100K + 1K} = \frac{100K}{101K} = \mathbf{0.99K}$$


3

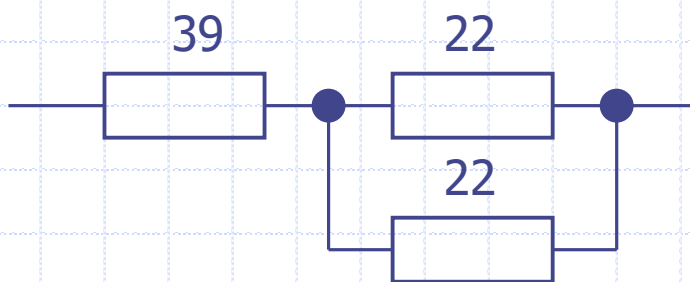

4

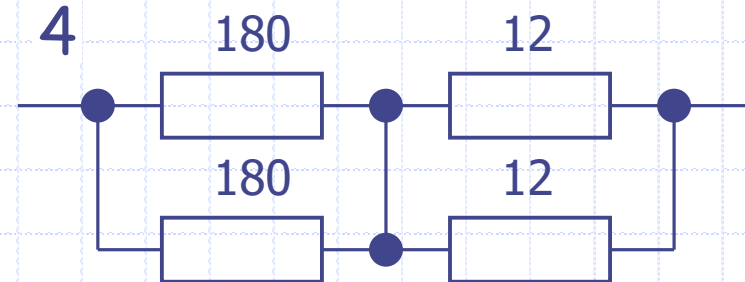


QUIK THINKAZ

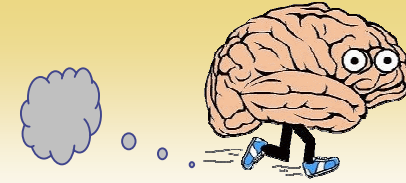


What is the overall value of each resistor network?

1

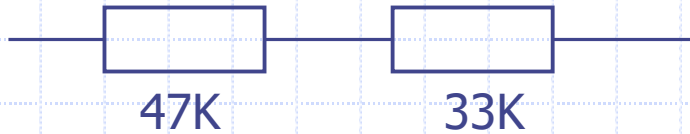


$$R_t = 47K + 33K = \mathbf{80K}$$

2

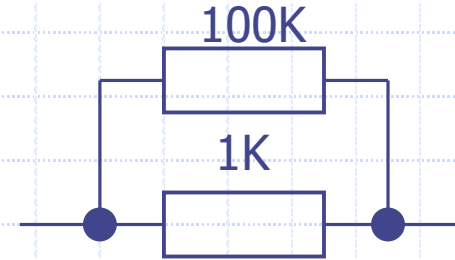


$$R_t = \frac{100K \times 1K}{100K + 1K} = \frac{100K}{101K} = \mathbf{0.99K}$$

3

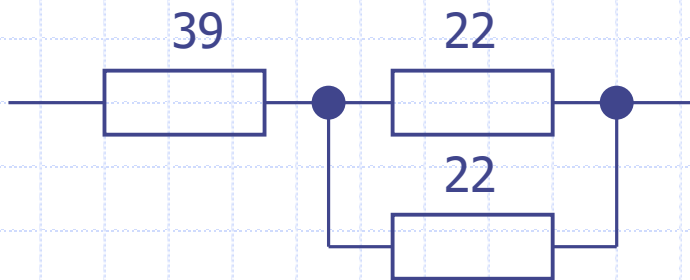


$$R_t = 39 + \frac{22 \times 22}{22 + 22} = 39 + \frac{484}{44} = 39 + 11 = \mathbf{50}$$

4

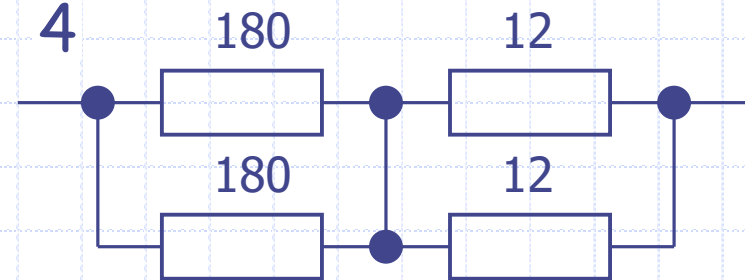


QUIK THINKAZ

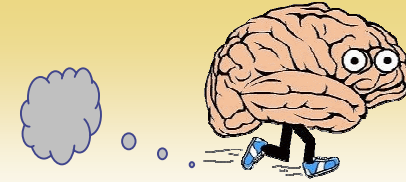


What is the overall value of each resistor network?

1

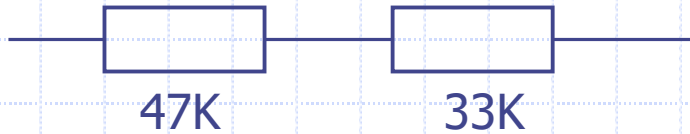


$$R_t = 47K + 33K = \mathbf{80K}$$

2

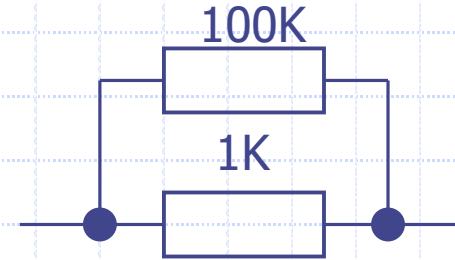


$$R_t = \frac{100K \times 1K}{100K + 1K} = \frac{100K}{101K} = \mathbf{0.99K}$$

3

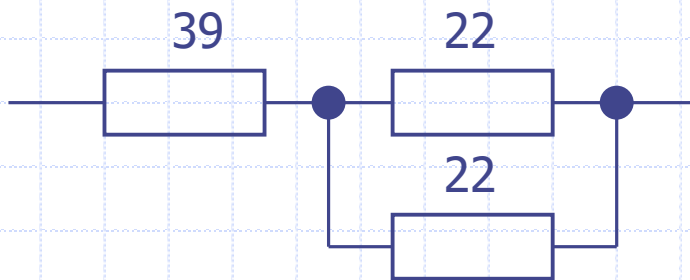

$$R_t = 39 + 11 = \mathbf{50}$$

4

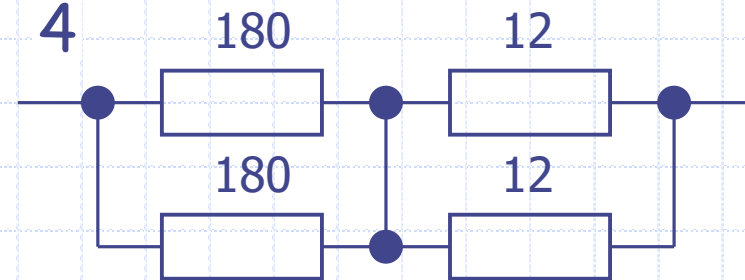

$$R_t = 90 + 6 = \mathbf{96}$$