
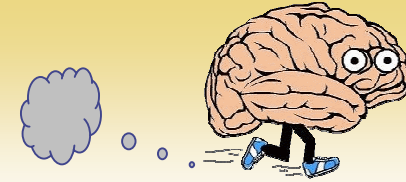


QUIK THINKAZ

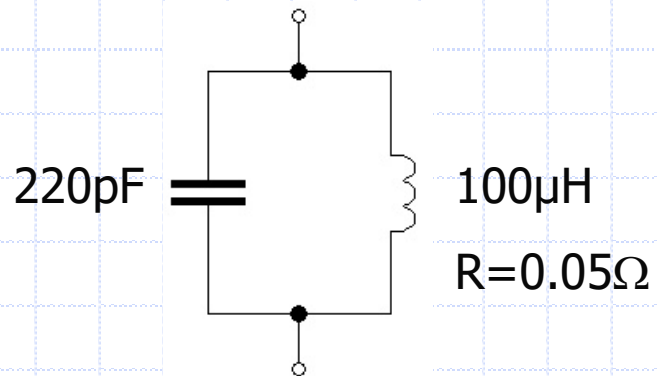


WORK OUT THE FOLLOWING:

- a) Tuned frequency
- b) Impedance at tuned frequency
- c) Half-width of filter



QUIK THINKAZ

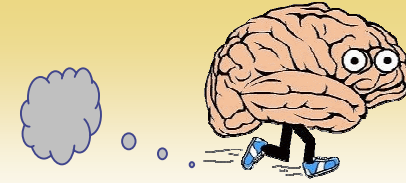

WORK OUT THE FOLLOWING:

a) Tuned frequency

$$f_o = 1 / 2\pi \sqrt{LC}$$

b) Impedance at tuned frequency

$$f_o = 1 / 2 \times 3.14 \times \sqrt{(100 \times 10^{-6} \times 220 \times 10^{-12})}$$


c) Half-width of filter

$$f_o = 1 / 6.28 \times \sqrt{(22 \times 10^{-15})}$$


$$f_o = 1 / 6.28 \times 148.3 \times 10^{-9}$$

$$f_o = 1 / 931.5 \times 10^{-9}$$
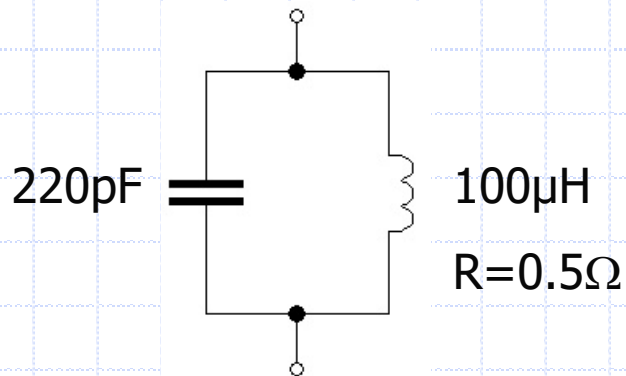
$$f_o = 1.07 \times 10^6 \text{ Hz or } 1.07 \text{ MHz}$$



QUIK THINKAZ

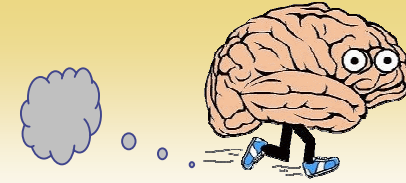

WORK OUT THE FOLLOWING:

a) Tuned frequency

$$f_0 = 1.07 \text{ MHz}$$

b) Impedance at tuned frequency


$$Z_0 = L / RC$$

c) Half-width of filter


$$Z_0 = 100 \times 10^{-6} / (0.5 \times 220 \times 10^{-12})$$

$$Z_0 = 100 \times 10^{-6} / 110 \times 10^{-12}$$
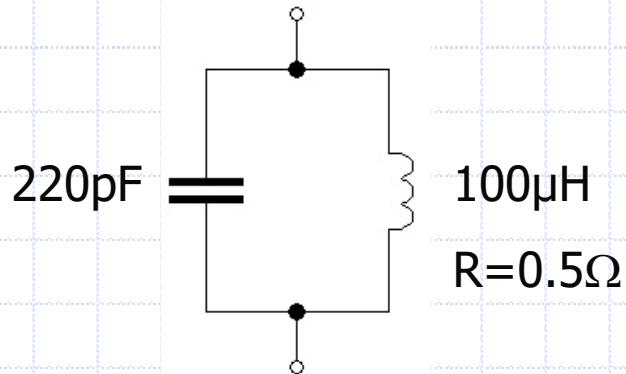
$$Z_0 = 909 \times 10^3 \Omega \text{ or } 909 \text{ K}\Omega$$



QUIK THINKAZ

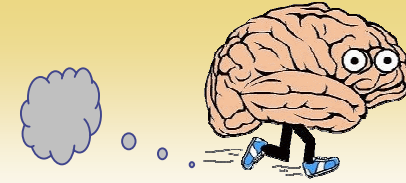

WORK OUT THE FOLLOWING:

a) Tuned frequency

$$f_o = 1.07 \text{ MHz}$$

b) Impedance at tuned frequency

$$Z_o = 909 \text{ K}\Omega$$


c) Half-width of filter

$$\delta f = R / 2 \pi L$$


$$\delta f = 0.5 / (2 \times 3.14 \times 100 \times 10^{-6})$$

$$\delta f = 0.5 / 628 \times 10^{-6}$$

$$\delta f = \mathbf{796 \text{ Hz}}$$

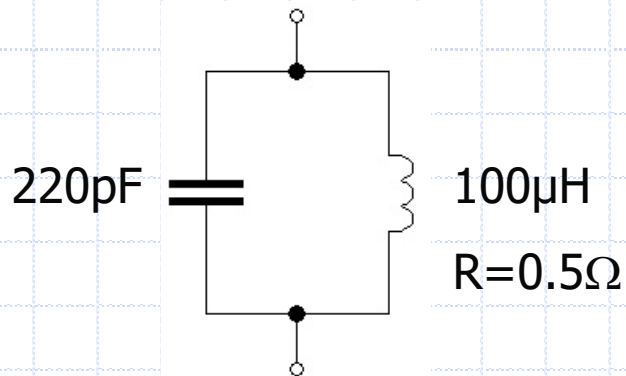

QUIK THINKAZ

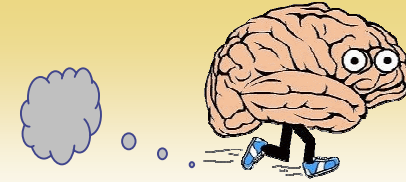

WORK OUT THE FOLLOWING:

- a) Tuned frequency $f_o = 1.07 \text{ MHz}$
- b) Impedance at tuned frequency $Z_o = 909 \text{ K}\Omega$
- c) Half-width of filter $\delta f = 796 \text{ Hz}$

